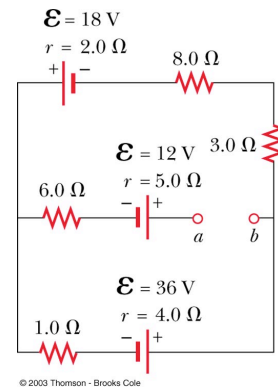


28. (a) Determine the potential difference  $\Delta V_{ab}$  for the circuit in Figure P18.28. Note that each battery has an internal resistance as indicated in the figure. (b) If points  $a$  and  $b$  are connected by a  $7.0\text{-}\Omega$  resistor, what is the current through this resistor?

18.28 (a) Since there is not a continuous path in the center branch, no current exists in that part of the circuit. Then, applying Kirchhoff's loop rule to the outer perimeter gives

$$+18\text{ V} + 36\text{ V} - [(1.0 + 4.0 + 3.0 + 8.0 + 2.0)\text{ }\Omega]I = 0$$

$$\text{or } I = \frac{54\text{ V}}{18\text{ }\Omega} = 3.0\text{ A}$$



Now, start at point  $b$  and go around the lower loop to point  $a$ , recording changes in potential to obtain

$$V_a - V_b = -36\text{ V} + (4.0\text{ }\Omega + 1.0\text{ }\Omega)(3.0\text{ A}) + (6.0\text{ }\Omega + 5.0\text{ }\Omega)(0) + 12\text{ V} = -9.0\text{ V},$$

$$\text{or } |\Delta V|_{ab} = \boxed{9.0\text{ V with point } b \text{ at a higher potential than } a}$$

(b) Assume currents as shown in the modified circuit. Applying Kirchhoff's loop rule to the upper loop gives

$$-(11)I + 12\text{ V} - (7.0)I - (13)I_1 + 18\text{ V} = 0$$

$$\text{or } 18I + 13I_1 = 30\text{ A} \quad (1)$$

For the lower loop, the loop rule yields

$$-(5.0)(I_1 - I) + 36\text{ V} + (7.0)I - 12\text{ V} + (11)I = 0,$$

$$\text{or } 23I - 5I_1 = -24\text{ A}. \quad (2)$$

Solving equations (1) and (2) simultaneously gives  $I_1 = 2.9\text{ A}$ , and

$$I = -0.42\text{ A}$$

Thus, the current in the  $7.0\text{-}\Omega$  resistor is  $\boxed{0.42\text{ A flowing from } b \text{ to } a}$ .